

ohm's law				
resistor #2				
reading	current I	voltage V		
1	0	0		
2	20	0.2		
3	30	0.3		
4	40	0.4		
5	52	0.5		
6	62	0.6		
resistor #7				
reading	current I	voltage V		
1	0	0		
2	12	0.2		
3	20	0.3		
4	26	0.4		
5	34	0.5		
6	40	0.6		
resistor #9				
reading	current I	voltage V		
1	0	0		
2	8	0.2		
3	12	0.3		
4	18	0.4		
5	22	0.5		
6	26	0.6		
#2 and #7 in series				
reading	current I	voltage V		
1	0	0		
2	8	0.2		
3	11	0.3		

4	16	0.4		
5	19	0.5		
6	24	0.6		
#7 and #9 in parallel				
reading	current (mA)	voltage v		
1	0	0		
2	22	0.2		
3	33	0.3		
4	44	0.4		
5	57	0.5		
6	70			